

[illegible][illegible]

3 3 Two lead telephone cable      Ú Ò (pretty poor Zener  
3 3 strung with parallel circuitry      3 huh?)  
3 3 in mind.      3 6V  
3 3      3

ÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄ(ÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄ)  
ÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄÄ

[illegible]

The 1.5K ohm pot on pin 8 and the \_\_\_\_\_ you want to be fancy, use a logic cap on pin 1 form a method of adjusting \_\_\_\_\_ gate. the "GAIN" of the amplifier from about 20 to about 200. (I used a single section like this in one of the local churches for the hard of hearing. I ran them off an amplifier used by the pastor. When the pastors amplifier was shut off and when adjusted to max, they kept complaining about picking up PBS.)

The 10K ohm pot on the inputs (pin 9) is what you use as the "VOLUME" control.

Transposing this stuff to ASCII aint the easiest thing I've ever done, so don't be surprized if I made some mistakes. (I'd be surprized if I didn't). If (when) you find any, please NET-MAIL me or .TIC me the correction(s). (9:1992/209 or 1:132/209) Thanks. I hope this helps.