

R T 3 3 3
B3 (6V)

A1 This potentiometer is connected to " S1 ".
Check Battery " B1 " for approx 2ma (milliampre) (.002 ampre) drain.
Check Battery " B2 " for approx 3 1/2 ma drain.
Adjust potentiometer on base of the NPN transistor untill the emitter diode draws approx 20 ma.

Phototransistor and Photodiode may be connected to the main assembly by a length of shielded mike cable.

Microphone is a crystal cartridge type (approx 1 inch diam.)

" R " is receive, " T " is transmit.
S2A-C need not be activated to receive.

Use proper Infra-red lenses. Glass is OPAQUE to I.R. and will SEVERELY degrade the performance of this device. Visible red may be used. Red filters over phototransistor will assist the rejection of light in the visible spectrum, and enhance the funtion of the amplifier.

Good luck. Be careful. I've done my best, but no promises.

(ps. Injection lasers may be substituted for the emitter in this circuit, with PROPER MODIFICATION).

□ □